EE3032 Introduction to VLSI Design—Homework 4

1. Draw the layout of the 3-bit ripple carry adder which you designed in Homework 3. Extract the netlist of the layout and measure the worst-case propagation delay and the average power consumption of the adder. Compare the measured delay and power (post-layout simulation results) with those shown in Homework 3 (pre-layout simulation results). (20 points)